
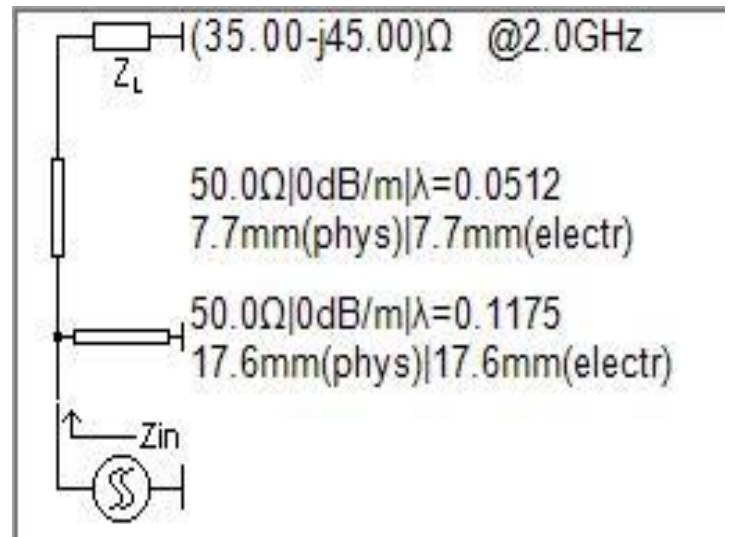


## Experiment No.8

### Design of an Short-Circuited Shunt Stub for Impedance Matching

#### Solution 1

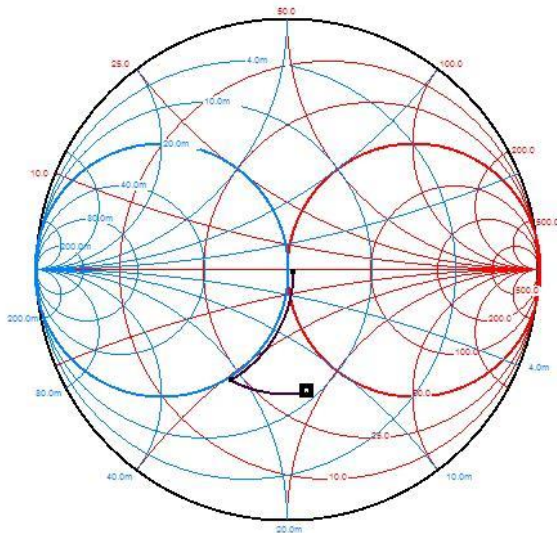

#### Solution 2

